

gangguan line to line (b:c):

$$I_a = 0$$

$$I_b = -I_c$$

$$V_b = V_c$$

$$I_{a0} = 0$$

$$I_{a1} = \frac{E_a}{Z_1 + Z_2} = \frac{1}{j0,10 + j0,15} = -j4 \text{ pu}$$

$$I_{a2} = -I_{a1} = j4 \text{ pu}$$

$$I_a = I_{a0} + I_{a1} + I_{a2} = 0 - j4 + j4 = 0$$

$$I_b = I_{a0} + a^2 I_{a1} + a I_{a2} = (a^2 - a) I_{a1}$$

$$= -j\sqrt{3} \frac{1}{j0,10 + j0,15} = +4\sqrt{3} \text{ pu}$$

$$= -6,928 \text{ pu} \quad -6,928 \text{ pu}$$

$$I_c = I_{a0} + a I_{a1} + a^2 I_{a2}$$

$$= (a - a^2) I_{a1} = -I_b = +6,928 \text{ pu}$$

$$I_{\text{dasar}} = \frac{30.000 \text{ KVA}}{\sqrt{3} \cdot 18 \text{ KV}} = 962,25 \text{ A}$$

Arus saluran :

$$I_a = 0$$

$$I_b = 6,928 \times 962,25 \text{ A} = -6666,468 \text{ A}$$

$$I_c = +6,928 \times 962,25 \text{ A} = +6666,468 \text{ A}$$

Arus gangguan :

$$I_f = I_b = -I_c = 6666,468 \text{ A}$$

Tegangan - tegangan saluran :

$$V_a = 2 \frac{Z_2}{Z_1 + Z_2} E_a = 2 \frac{j0,15}{j0,10 + j0,15} \cdot 1 = 1,2 \text{ pu}$$


$$= 1,2 \times 18 \text{ KV} = 21,6 \text{ KV}$$

$$V_b = -\frac{Z_2}{Z_1 + Z_2} E_a = -\frac{j0,15}{j0,10 + j0,15} \cdot 1 = -0,6 \text{ pu}$$

$$= -0,6 \times 18 \text{ KV} = -10,8 \text{ KV}$$

$$V_c = V_b = -10,8 \text{ KV}$$

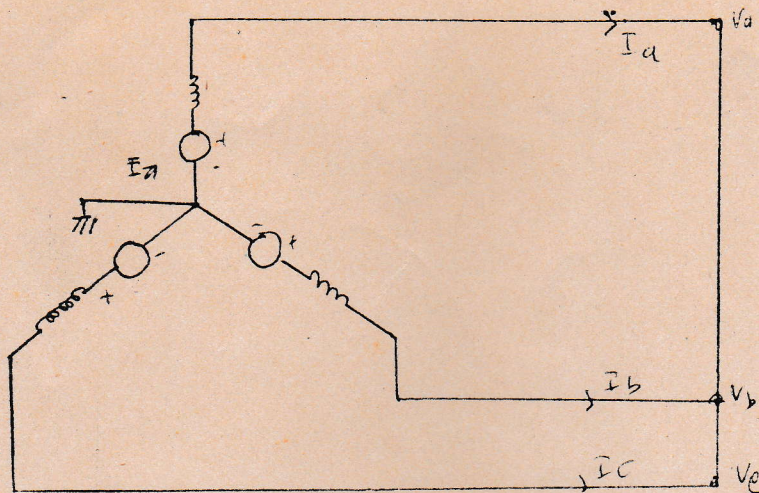1.5. GANGGUAN 3 PHASA (THREE PHASE FAULT)



Persamaan - persamaan
pada titik gangguan

$$V_a - V_b = 0 \quad (1)$$

$$V_a = V_b$$

$$V_a - V_c = 0 \quad (2)$$

$$V_a = V_c$$

$$I_a + I_b + I_c = 0 \quad (3)$$

dan (1) & (2)

$$V_{a0} = \frac{1}{3} (V_a + V_b + V_c) = \frac{3V_a}{3} = V_a$$

$$V_{a1} = \frac{1}{3} (V_a + \alpha V_b + \alpha^2 V_c) = \frac{1}{3} (1 + \alpha + \alpha^2) V_a = 0$$

$$V_{a2} = \frac{1}{3} (V_a + \alpha^2 V_b + \alpha V_c) = \frac{1}{3} (1 + \alpha^2 + \alpha) V_a = 0$$

dan (3)

$$I_{a0} = \frac{1}{3} (I_a + I_b + I_c) = \frac{1}{3} \cdot 0 = 0$$

dan persamaan umum:


$$V_{a1} = E_a - I_{a1} z_1 = 0$$

$$E_a = I_{a1} z_1$$

$$I_{a1} = \frac{E_a}{z_1}$$

$$V_{a2} = -I_{a2} z_2 = 0$$

$$I_{a2} = 0$$

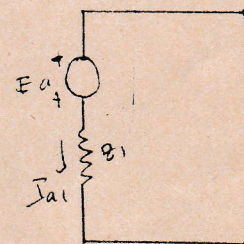

dan - dan salinan:

$$I_a = I_{a0} + I_{a1} + I_{a2} = 0 + \frac{E_a}{z_1} + 0 = \frac{E_a}{z_1}$$

$$I_b = I_{a0} + \alpha^2 I_{a1} + \alpha I_{a2} = 0 + \alpha^2 \frac{E_a}{z_1} + 0 = \alpha^2 \frac{E_a}{z_1}$$

$$I_c = I_{a0} + \alpha I_{a1} + \alpha^2 I_{a2} = 0 + \alpha \frac{E_a}{z_1} + 0 = \alpha \frac{E_a}{z_1}$$

dan gangguan

$$I_f = I_{a1} = \frac{E_a}{z_1}$$

tegangan - tegangan salinan: Kalau $z_0 = \infty$ terbungga $\rightarrow V_{a0} = 0$, maka

$$V_a = V_{a0} + V_{a1} + V_{a2} = V_{a0} + 0 + 0 = V_{a0} = 0$$


$$V_b = V_{a0} + \alpha^2 V_{a1} + \alpha V_{a2} = V_{a0} + 0 = V_{a0} = 0$$

$$V_c = V_{a0} + \alpha V_{a1} + \alpha^2 V_{a2} = V_{a0} + 0 = V_{a0} = 0$$

Contoh : I.5.

Hitunglah arus-arus sub peralihan pada keadaan sub peralihan bila suatu gangguan 3 phase terjadi pada generator yang telah diuraikan dalam contoh I.4.

Jawab :

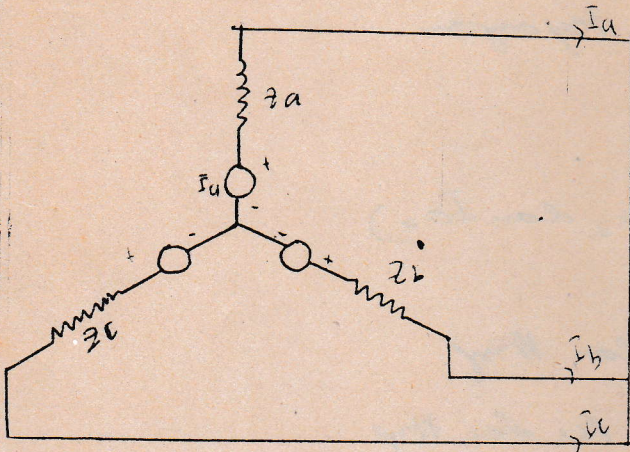

$$Z_1 = j0,10 \text{ pu}$$

$$Z_2 = j0,15 \text{ pu}$$

$$Z_0 = j0,05 \text{ pu}$$

$$I_a = 1 \text{ pu}$$

$$I_{\text{dasar}} = \frac{30.000 \text{ KVA}}{\sqrt{3} \cdot 18 \text{ KV}} = 962,25 \text{ A}$$

$$I_{a1} = \frac{E_a}{Z_1} = \frac{1}{j0,10} = -j10 \text{ pu}$$

$$I_{a2} = I_{a0} = 0$$

$$I_a = I_{a1} + I_{a2} + I_{a0} = -j10 \text{ pu}$$


$$I_a \text{ sebenarnya} = 10 \times 962,25 \text{ A} = 9622,5 \text{ A}$$

$$I_b = a^2 I_{a1} = (-0,5 - j0,866) \cdot -j10 = (5j - 8,66) \text{ pu}$$

$$I_b \text{ sebenarnya} = 10 \angle 150^\circ \times 962,25 \text{ A} = 9622,5 \angle 150^\circ \text{ A}$$


$$I_c = a I_{a1} = (-0,5 + j0,866) \cdot -j10 = j5 + 8,66 \text{ pu}$$
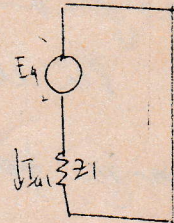
$$I_c \text{ sebenarnya} = 10 \angle 30^\circ \times 962,25 \text{ A} = 9622,5 \angle 30^\circ \text{ A}$$



II. GENERATOR NETRALNYA DITANAHKAN MELALUI IMPEDANSI REAKTOR

105

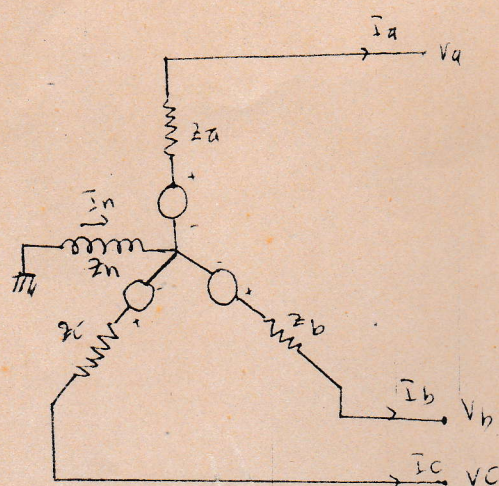

$$V_{a1} = E_a - I_{a1} z_1$$

$$V_{a2} = 0 - I_{a2} z_2$$

$$V_{a0} = 0 - I_{a0} z_0' - I_n z_n$$

$$I_n = I_a + I_b + I_c$$

$$\begin{aligned} V_{a0} &= -I_{a0} z_0' - (I_a + I_b + I_c) z_n \\ &= -I_{a0} z_0' - 3I_{a0} z_n \\ &= -I_{a0} (z_0' + 3z_n) = -I_{a0} z_0 \end{aligned}$$


$$z_0 = z_0' + 3z_n$$

z_0' = impedansi urutan nol antara netral dan titik gangguan

z_0 = impedansi urutan nol antara titik gangguan dan tanah

z_n = impedansi reaktansi netral generator ke tanah.

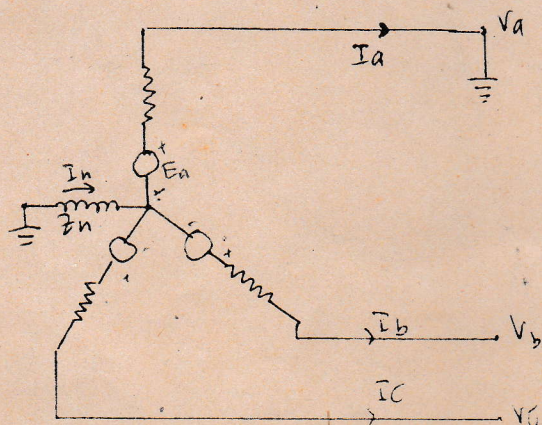II.1. GANGGUAN SATU SALURAN KE TANAH (PHASE A) (SINGLE LINE TO GROUND FAULT)



Persamaan - persamaan keadaan pada titik gangguan :

$$V_a = 0 \quad (1)$$

$$I_b = 0 \quad (2)$$

$$I_c = 0 \quad (3)$$

dan (2) & (3) diperoleh :

$$I_{a0} = \frac{1}{3} (I_a + I_b + I_c) = \frac{1}{3} (I_a + 0 + 0) = \frac{1}{3} I_a$$

$$I_{a1} = \frac{1}{3} (I_a + aI_b + a^2I_c) = \frac{1}{3} (I_a + 0 + 0) = \frac{1}{3} I_a$$

$$I_{a2} = \frac{1}{3} (I_a + a^2I_b + aI_c) = \frac{1}{3} (I_a + 0 + 0) = \frac{1}{3} I_a$$

$$\therefore I_{a0} = I_{a1} = I_{a2} = \frac{1}{3} I_a$$

dan (1)

$$V_a = V_{a1} + V_{a2} + V_{a0} = 0$$

$$\begin{aligned} V_{a1} &= -(V_{a0} + V_{a2}) \\ &= -(-I_{a0}z_0' - I_n z_n - I_{a2} z_2) \\ &= I_{a0}z_0' + I_n z_n + I_{a2} z_2 \\ &= I_{a0}z_0' + 3I_{a0}z_n + I_{a2} z_2 \\ &= I_{a0}(z_0' + 3z_n) + I_{a2} z_2 \\ &= I_{a1}(z_0' + 3z_n + z_2) \end{aligned}$$

Persamaan umum

$$V_{a1} = E_a - I_{a1} z_1$$


maka

$$E_a - I_{a1} z_1 = I_{a1}(z_0' + 3z_n + z_2)$$

$$I_{a1}(z_0' + 3z_n + z_2 + z_1) = E_a$$

$$I_{a1} = \frac{E_a}{(z_0' + 3z_n) + z_2 + z_1} = \frac{E_a}{z_0 + z_1 + z_2} \rightarrow I_{a1} = I_{a2} = I_{a0}$$

Rangkaian ekuivalennya :

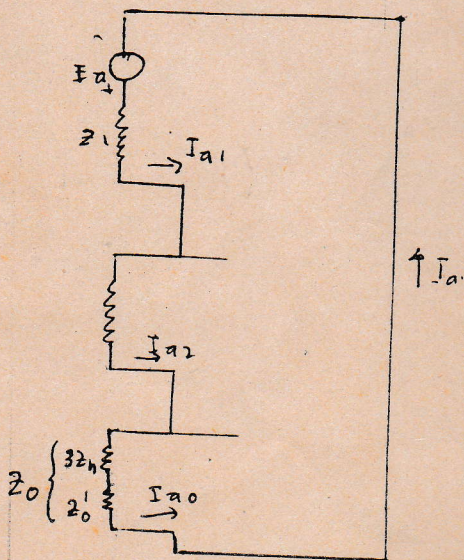

$$I_{a0} = I_{a1} = I_{a2} = \frac{E_a}{(z_0' + 3z_n) + z_2 + z_1}$$

$$\begin{aligned} V_{a0} &= -I_{a0}z_0 = -I_{a0}(z_0' + 3z_n) \\ &= -\frac{z_0' + 3z_n}{(z_0' + 3z_n) + z_2 + z_1} E_a \cdot I_{a0} \end{aligned}$$

$$\begin{aligned} V_{a1} &= E_a - I_{a1} z_1 \\ &= E_a - \frac{z_1}{(z_0' + 3z_n) + z_2 + z_1} E_a \\ &= \frac{z_0' + 3z_n + z_2}{z_0' + 3z_n + z_2 + z_1} E_a \end{aligned}$$

$$\begin{aligned} V_{a2} &= -I_{a2} z_2 \\ &= -\frac{z_2}{z_0' + 3z_n + z_2 + z_1} E_a \end{aligned}$$

Arus gangguan : $I_f = I_a$

$$I_a = I_{a0} + I_{a1} + I_{a2} = \frac{3 E_a}{z_0' + 3z_n + z_2 + z_1}$$

$$z_0 = z_0' + 3z_n$$